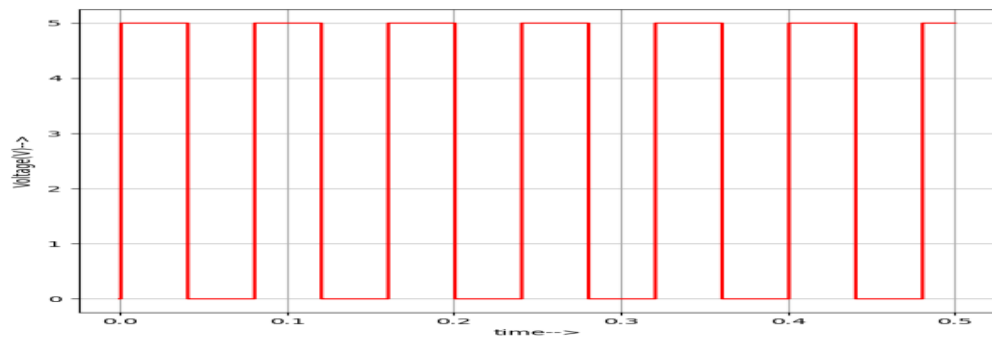





The plot shows a square wave signal. The voltage is 5V for the first half of each 0.05s period and 0V for the second half. The period of the signal is 0.05s.


(a): Clock applied to first JK Flip-flop



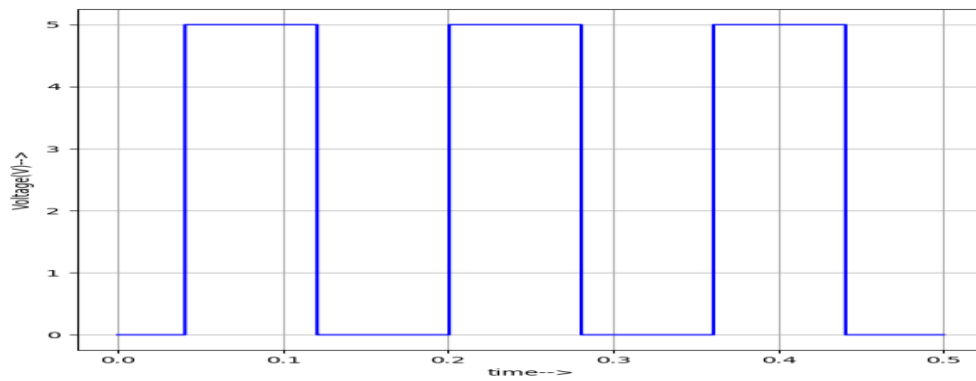
(b): LSB (Bo or Q0) is the output of 2-bit asynchronous counter from first JK Flip-flop



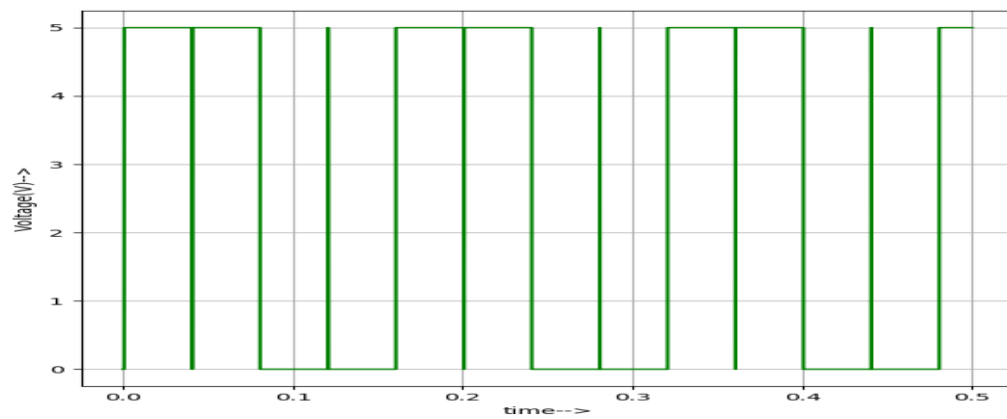(c): MSB (B1or Q1) is the output of the 2-bit asynchronous counter from the second JK Flip-flop



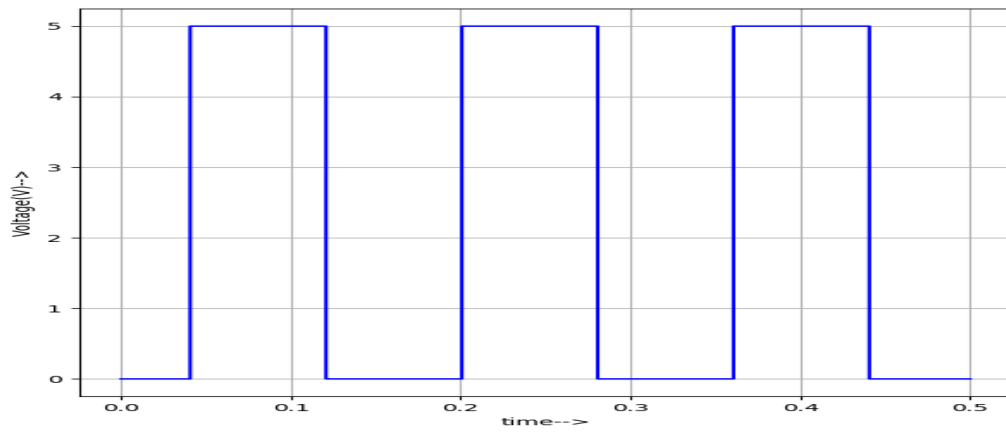(d): LSB (Go) is the output of 2-bit Binary to Gray Code Converter i.e. $B_0 \text{ XOR } B_1$



(e): MSB (G1) is the output of 2-bit Binary to Gray Code Converter i.e. $G1 = B1$)